LESSON 7: PUSH BUTTON

INTRODUCTION


Push buttons or switches connect two points in a circuit when you press them. This example turns on one led when the button pressed, and off when the button unpressed.

COMPONENTS

- Arduino uno
- Breadboard
- LED
- 220 Ohm & 10K Ohm resistor
- Push button
- Jumper wire

CONNECTION

STEP 1: The circuit

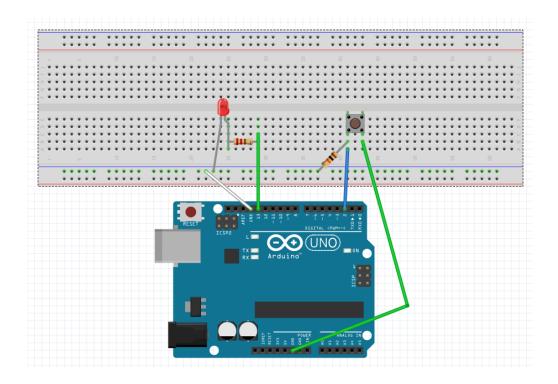


- Connect one of the Arduino GND pins to one of the long power rails on the breadboard

 this will be the ground rail.
- 2. Connect the short leg of the LED to this same ground rail on the breadboard then connect the long leg to a row on the breadboard.
- 3. Connect the 220-ohm resistor to pin 13.
- 4. Place the pushbutton on the breadboard. Most buttons will straddle the center trench on the breadboard.
- 5. Connect a jumper wire from the 5-volt pin to one side of the pushbutton.
- 6. Connect a jumper wire from pin 2 to the other side of the pushbutton.
- 7. Connect one side of the 10k resistor from the ground rail on the breadboard to the other side to the pushbutton on the same side that pin 2 connects.


STEP 2: Program

```
// constants won't change. They're used here to
// set pin numbers:
const int buttonPin = 2; // the number of the pushbutton pin
const int ledPin = 13; // the number of the LED pin
// variables will change:
int buttonState = 0;
                       // variable for reading the pushbutton status
void setup() {
// initialize the LED pin as an output:
pinMode(ledPin, OUTPUT);
// initialize the pushbutton pin as an input:
pinMode(buttonPin, INPUT);
}
void loop() {
// read the state of the pushbutton value:
buttonState = digitalRead(buttonPin);
// check if the pushbutton is pressed.
// if it is, the buttonState is HIGH:
if (buttonState == HIGH) {
 // turn LED on:
  digitalWrite(ledPin, HIGH);
} else {
  // turn LED off:
  digitalWrite(ledPin, LOW);
}
```

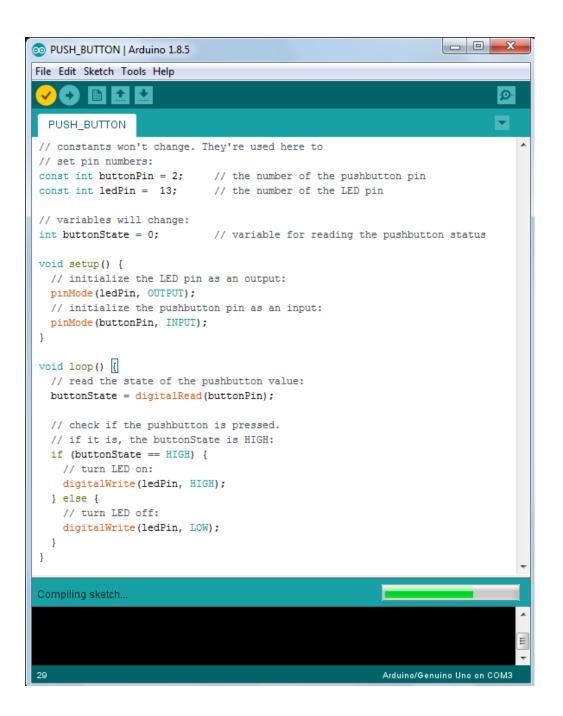STEP 3: Compile the code. Click the Verify button on the top left. It should turn orange and then back to blue.



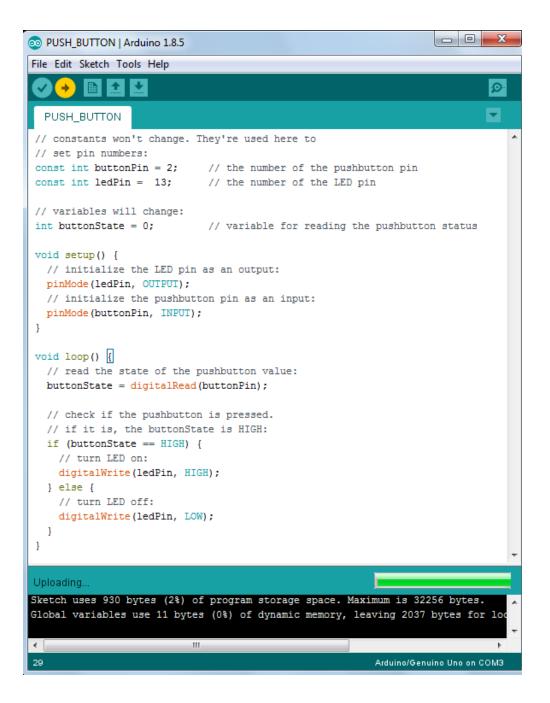STEP 4: Upload the sketch to Arduino UNO board. Click the Upload button. It will also turn orange and then blue once the sketch has finished uploading to your Arduino board.



RESULT: When the pushbutton is open (unpressed) there is no connection between the two legs of the pushbutton, so the pin is connected to ground (through the pull-down resistor) and we read a LOW. When the button is closed (pressed), it makes a connection between its two legs, connecting the pin to 5 volts, so that we read a HIGH.