LESSON 5: LDR

INTRODUCTION

An LDR is a component that has a (variable) resistance that changes with the light intensity that falls upon it. This allows them to be used in light sensing circuits. In this project we will use arduino uno. This is simple arduino project; turn on LED when it's dark and turn off when is light.

COMPONENTS

- Arduino Uno
- LED
- LDR (photoresistor)
- 220Ω and 10k ohm resistors
- Jumper wires
- Breadboard

CONNECTION

STEP 1: LED Connection







- 1. LED attach to board
- 2. Resistor (220 ohm) one leg attach to LED long leg
- 3. The green wire attach to resistor's empty leg
- 4. The brown wire attach o LED short leg

STEP 2: LDR Connection





- 1. LDR attach to board
- 2. Resistor (10k ohm) attach to LDR one leg
- 3. The purple wire attach to LDR other (empty) leg
- 4. The yellow wire attach to LDR and resistor same column
- 5. The white wire attach to resistor empty leg

STEP 3: Arduino Connection



- 1. The green wire connect to digital 13 from resistor leg
- 2. The brown wire connect to GND from LED short ${\sf leg}$
- 3. The purple wire connect to +5V from LDR
- 4. The yellow wire connect to A0
- 5. The white wire connect to GND

STEP 4: Program

```
//set pin numbers
//const won't change
const int ledPin = 13; //the number of the LED pin
const int ldrPin = A0; //the number of the LDR pin
void setup() {
Serial.begin(9600);
pinMode(ledPin, OUTPUT); //initialize the LED pin as an output
pinMode(ldrPin, INPUT); //initialize the LDR as an input
}
void loop() {
int ldrStatus = analogRead(ldrPin); //read the status of the LDR value
//check if the LDR status is <= 300
//if it is, the LED is HIGH
if (ldrStatus <= 300) {
digitalWrite(ledPin, HIGH); //turn LED on
Serial.println("LDR is DARK, LED is ON");
}
else {
 digitalWrite(ledPin, LOW); //turn LED off
Serial.println("-----");
}
```

STEP 5: Compile the code



STEP 6: Upload the sketch to the Arduino UNO.



RESULT: LED turn on when it's dark and turn off when is light.

💿 COM3 (Arduino/Genuino Uno)	
	Send
LDR is DARK, LED is ON	*
LDR is DARK, LED is ON	
LDR is DARK, LED is ON	
LDR is DARK, LED is ON	
LDR is DARK, LED is ON	
LDR is DARK, LED is ON	
LDR is DARK, LED is ON	
LDR is DARK, LED is ON	
LDR is DARK, LED is ON	
LDR is DARK, LED is ON	
LDR is DARK, LED is ON	
LDR is DARK, LED is ON	
LDR is DARK, LED is ON	
LDR is DARK, LED is ON	
LDR is DARK, LED is ON	
LDR is DARK, LED is ON	
LDR is DARK, LED is ON	
LDR is DARK, LED is ON	
LDR is DARK, LED is ON	
LDR is DARK, LED is ON	
LDR is DARK, LED is ON	
LDR is DARK, LED is ON	
LDR is DARK, LED is ON	
LDR is DARK, LED is ON	
LDR is DARK, LED is ON	
LDR is DARK, LED is ON	
LDR is DARK, LED is ON	
LDR is DARK, LED is ON	_
LDR is DARK, LED is ON	E
LDR is	-
< III	۱.
V Autoscroll No line ending	aud 👻 Clear output



💿 COM3 (Arduino/Genuino Uno)	
	Send
LDR is DARK, LED is ON	
LDR is DARK, LED is ON	
LDR is DARK, LED is ON	
LDR is DARK, LED is ON	
LDR is DARK, LED is ON	
LDR is DARK, LED is ON	
LDR is DARK, LED is ON	
LDR is DARK, LED is ON	
LDR is DARK, LED is ON	
LDR is DARK, LED is ON	
LDR is DARK, LED is ON	
LDR is DARK, LED is ON	
<	•
▼ Autoscroll No line ending ▼ 9600	baud 👻 Clear output